



University of San Carlos | Department of
COMPUTER ENGINEERING

CPE 3101L – Introduction to HDL

Unit 4: Dataflow Modeling of Combinational Circuits


Lecture 1

Outline

- Dataflow Modeling of Combinational Circuits
- Verilog HDL Operators
- Continuous Assignment: ***Assign*** Statement
- Conditional Assignment
- Synthesis of z and x values
- Concatenation and Replication
- Constants and Parameters

Combinational Logic in Verilog

 - To create the HDL model of combinational circuits:
- Structural modeling (*Units 2-3*)
 - Gate primitives, UDPs, other HDL modules
 - Needs schematic or truth tables or other HDL modules
- Dataflow modeling (*Unit 4*)
 - Needs Boolean equations
- Behavioral modeling (*Unit 5*)
 - Needs behavior or functionality of the circuit
 - *More frequently used in sequential logic (Unit 6)*



Dataflow Modeling of Combinational Circuits

- **Dataflow modeling** uses a **number of operators that act on binary operands** to produce a binary result.
- **Dataflow HDL models** describe combinational circuits by their ***function*** rather than their gate structure.
 - Boolean function
 - Logical function


Verilog HDL Operators

	Symbol	Operation	Symbol	Operation	
Bitwise	&	Bitwise AND	&&	Logical AND	Logical
		Bitwise OR		Logical OR	
	^	Bitwise XOR			
	~	Bitwise NOT	!	Logical NOT	
Equality	==	Equality	!=	Inequality	
	>	Greater than	<	Less than	
	>=	Greater than or equal	<=	Less than or equal	
Arithmetic	+	Binary addition	-	Binary subtraction	
	%	Modulus	**	Exponentiation	
Shift	>>	Logical right shift	>>>	Arithmetic right shift	
	<<	Logical left shift	<<<	Arithmetic left shift	
Concatenation	{ }	Concatenation	{ { } }	Replication	
Conditional	?:	Conditional			

*Use the bitwise operations to describe arithmetic operations and logical operators for logical operations.

Continuous Assignment

 
- *Assign* keyword is a straightforward way of assigning a combinational logic function to a net (*wire*)
- Use of operators is allowed in an *assign* statement
- Example:



Structural model with gate primitives

```

 wire  x, y;
and    u1 (x, a, b);
or     u2 (y, x, c);
    
```



Dataflow model using assign

```


wire  y;
assign y = (a & b) | c;
    
```

Example 1: Full Adder

- Create a Verilog [dataflow description](#) of a full adder.

- Specifications:**

- Inputs: x, y, z
- Outputs: C, S

 


x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = z \oplus (x \oplus y)$$

$$C = xy + xz + yz$$

Example 1: Design Entry (Full Adder)

- Entity Diagram:

 

- Logic Function/s:

$$S = z \oplus (x \oplus y)$$

$$C = xy + xz + yz$$

- Verilog HDL Description:


```
// Dataflow model of a Full Adder
module FullAdder (
    input    x, y, z,
    output   C, S
);

    assign S = x ^ y ^ z; // S = z ^ (x ^ y);
    assign C = (x & y) | (x & z) | (y & z);
endmodule
```


Example 1: Synthesized Design (Full Adder)

- RTL Schematic View:

Total logic elements	2
Total registers	0
Total pins	5

 

Example 1: Testbench File (Full Adder)

```
// Testbench file of Dataflow Full Adder

`timescale 1 ns / 1 ps
module tb_FullAdder ();

    // declare inputs as reg types
    reg    x, y, z;

    // outputs as wire types
    wire   C, S;

    // instantiate UUT
    FullAdder UUT ( .x(x), .y(y), .z(z), .C(C), .S(S) );

    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);

        x = 1'b0;    y = 1'b0;    z = 1'b0;    #10
        x = 1'b0;    y = 1'b0;    z = 1'b1;    #10
        x = 1'b0;    y = 1'b1;    z = 1'b0;    #10
        x = 1'b0;    y = 1'b1;    z = 1'b1;    #10

        x = 1'b1;    y = 1'b0;    z = 1'b0;    #10
        x = 1'b1;    y = 1'b0;    z = 1'b1;    #10
        x = 1'b1;    y = 1'b1;    z = 1'b0;    #10
        x = 1'b1;    y = 1'b1;    z = 1'b1;    #10

        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial begin
        $monitor("Time = %2d ns\t xyz = %b%b%b\t C = %b\t S = %b", $time, x, y, z, C, S);
    end
endmodule
```


Example 1: Simulation (Full Adder)

- Standard Output:

```
# Starting simulation at 0 ns...
# Time = 0 ns   xyz = 000   C = 0   S = 0
# Time = 10 ns  xyz = 001   C = 0   S = 1
# Time = 20 ns  xyz = 010   C = 0   S = 1
# Time = 30 ns  xyz = 011   C = 1   S = 0
# Time = 40 ns  xyz = 100   C = 0   S = 1
# Time = 50 ns  xyz = 101   C = 1   S = 0
# Time = 60 ns  xyz = 110   C = 1   S = 0
# Time = 70 ns  xyz = 111   C = 1   S = 1
# Finished simulation at 80 ns.
```

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Waveform:

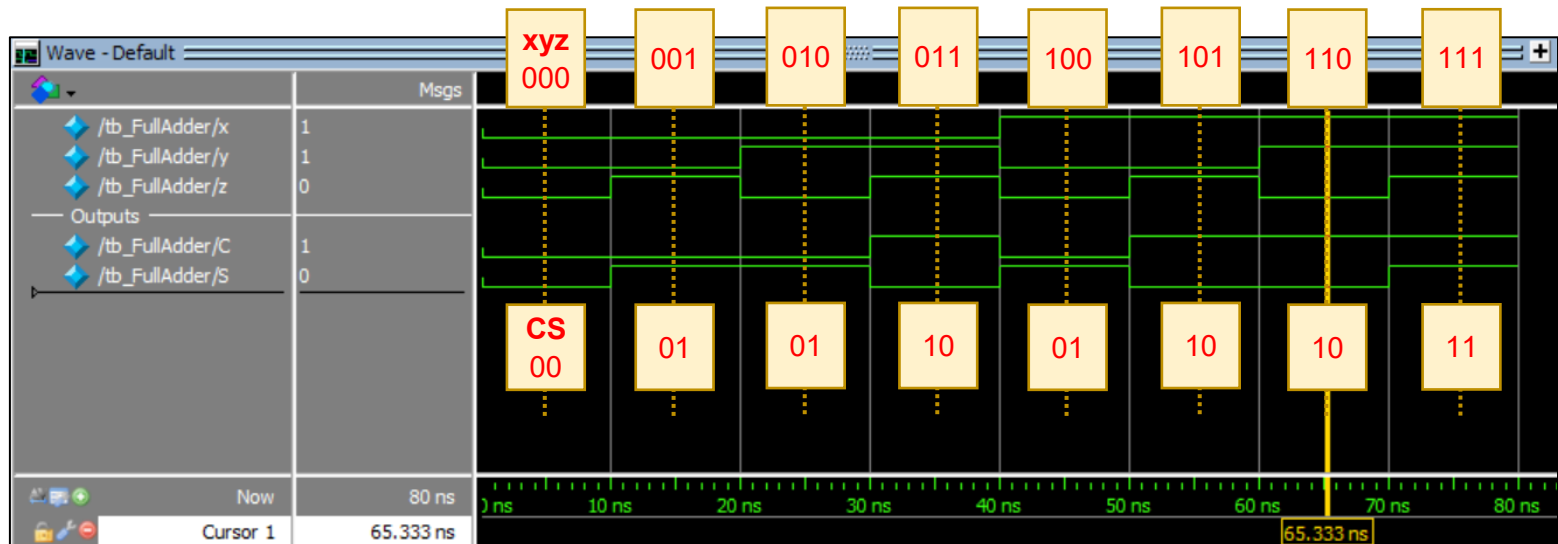


Conditional Assignment

- Assigned value is dependent on the evaluation of a condition
- Uses the *conditional operator* (?) which takes 3 operands:

`[condition] ? [true_expression] : [false_expression];`

 - Condition (Boolean expression) is evaluated:
 - If result is logic 1, *true_expression* is evaluated;
 - Else, *false_expression* is evaluated
- Can be used with *assign* statement, but not limited to it
- Example: Modeling a 2x1 mux (3 assign statement variations)





```
assign Y = (S==0) ? I[0] : I[1];  
assign Y = (S==1) ? I[1] : I[0];  
assign Y = (S)      ? I[1] : I[0];
```

Conditional Assignment


- Conditional assignments may also be cascaded or nested
- Less lines of code but can be harder to read
- Synthesized hardware of conditional assignments infers 2x1 multiplexers

- Example:

  

Synthesis of z

 
- The **z** value implies **high impedance** or an **open circuit**.
- Not a normal logic value (like 1 or 0)
- Can only be synthesized by a **tri-state buffer**



Output Enable (oe)	y
0	z
1	a_in

- Dataflow model of a tri-state buffer:

```
assign y = (oe) ? a_in : 1'bz;
```

 

Synthesis of x

- Don't care values (x) are assigned when input patterns/ combinations never occur, thus the output value is irrelevant.

- Example:

Input i	Output y
00	0
01	1
10	1
11	x

```
assign y = (i == 2'b00) ? 1'b0 :
           (i == 2'b01) ? 1'b1 :
           (i == 2'b10) ? 1'b1 :
                    1'bx; // i == 2'b11
```

- This approach helps minimize the circuit but it introduces a discrepancy between simulation and synthesis:
 - Simulation:** x is a unique value (rather than 0 or 1)
 - Synthesis:** x may either be 0 or 1 (not x)

This input pattern (11) never occurs so don't care value (x) is assigned to output y for optimization (i.e. K-maps, etc.)

Concatenation

- Multiple signals may be concatenated to form a larger signal (*larger array*)

- Uses the **concatenation operator** (`{ }`)

```
assign [large_signal] = { [sig1], [sig2], ... };
```

- Implementation involves **reconnection** (*rewiring*) of input/output signals
- Useful for **transforming individual signals into buses**
- Example:



```
wire [2:0] x;  
assign x = {q, r, s};  
sub2 u1 ( .b(x), .w(n) );
```


Concatenation

- **Syntax:** `assign [large_signal] = { [sig1], [sig2], ... };`
- Examples:

```
wire a1;
wire [3:0] a4;
wire [7:0] b8, c8, d8;

assign b8 = {a4, a4};
assign c8 = {a1, a1, a4, 2'b00};
assign d8 = {b8[3:0], c8[3:0]};
```

```
wire [7:0] a, rot, shl, shr;

assign rot = {a[6:0], a[7]}; //rotate a once to the left
assign shl = {a[6:0], 1'b0}; //logic shift left once (multiply a by 2)
assign shr = {1'b0, a[7:1]}; //logic shift right once (divide a by 2)
```

Replication

- Used to **replicate a signal** a finite number of times
- The **concatenation operator** (**$\{ N\} \}$**) replicates the enclosed signal
- The **replication constant** (**N**) specifies the number of replications:

```
assign [large_signal] = { N { [signal] } };
```

- Useful for **padding bits** or for **sign-extension**
- Example: **2's complement sign-extension** from 8-bit to 32-bit

```
wire [7:0] x;  
wire [31:0] y;  
  
assign y = { { 24 {x[7]} }, x }; // sign-extend MSB
```


Example 2: 4-bit Binary Adder

- Create a Verilog dataflow description of a 4-bit binary adder.

- Specifications:

- Inputs: A [3:0], B [3:0], C_in
- Outputs: C_out, Sum [3:0]

- Design Entry:

 

```
// Dataflow model of a 4-bit Binary Adder
module BinAdder_4bit (
    output [3:0] Sum,
    output C_out,
    input [3:0] A, B,
    input C_in
);
    assign {C_out, Sum} = A + B + C_in;
endmodule
```

Example 2: Testbench (Binary Adder)

```
// Testbench file of Dataflow Binary Adder

`timescale 1 ns / 1 ps
module tb_BinAdder_4bit ();

    // declare inputs as reg types
    reg [3:0] A, B;
    reg      C_in;

    // outputs as wire types
    wire [3:0] Sum;
    wire      C_out;

    // instantiate UUT
    BinAdder_4bit UUT ( .A(A), .B(B), .C_in(C_in), .Sum(Sum), .C_out(C_out) );


    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);
        A = 4'd0;   B = 4'd0;   C_in = 1'b0;   #5
        A = 4'd0;   B = 4'd0;   C_in = 1'b1;   #5
        A = 4'd5;   B = 4'd10;  C_in = 1'b0;   #5
        A = 4'd3;   B = 4'd4;   C_in = 1'b1;   #5
        A = 4'd11;  B = 4'd2;   C_in = 1'b0;   #5
        A = 4'd14;  B = 4'd15;  C_in = 1'b1;   #5
        A = 4'd15;  B = 4'd15;  C_in = 1'b0;   #5
        A = 4'd6;   B = 4'd9;   C_in = 1'b1;   #5

        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial begin
        $monitor("Time = %2d ns\t A = %b\t B = %b\t C_in = %b\t C_out = %b\t Sum = %b\t = %d\t {C_out, Sum} = %2d",
            $time, A, A, B, B, C_in, C_out, Sum, Sum, (Sum+(C_out*(16))) );
    end
endmodule
```

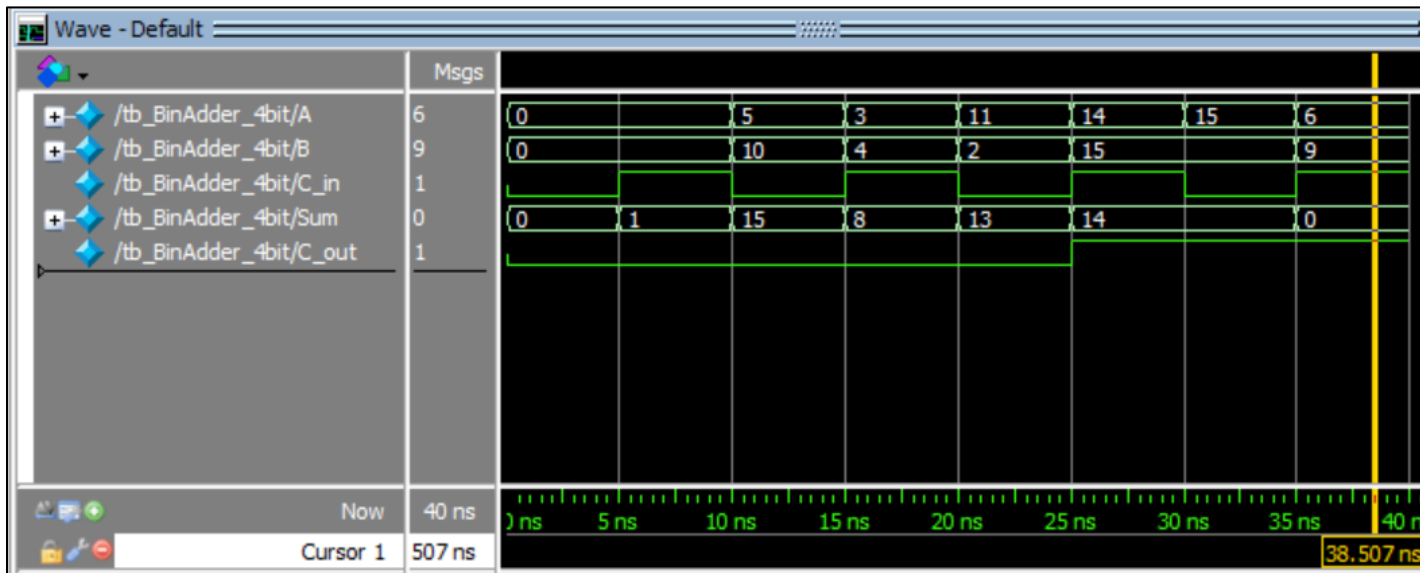Example 2: Simulation (Binary Adder)


```
# Starting simulation at 0 ns...
# Time = 0 ns  A = 0000 = 0  B = 0000 = 0  C_in = 0  C_out = 0  Sum = 0000 = 0  {C_out, Sum} = 0
# Time = 5 ns  A = 0000 = 0  B = 0000 = 0  C_in = 1  C_out = 0  Sum = 0001 = 1  {C_out, Sum} = 1
# Time = 10 ns A = 0101 = 5  B = 1010 = 10 C_in = 0  C_out = 0  Sum = 1111 = 15 {C_out, Sum} = 15
# Time = 15 ns A = 0011 = 3  B = 0100 = 4  C_in = 1  C_out = 0  Sum = 1000 = 8  {C_out, Sum} = 8
# Time = 20 ns A = 1011 = 11 B = 0010 = 2  C_in = 0  C_out = 0  Sum = 1101 = 13 {C_out, Sum} = 13
# Time = 25 ns A = 1110 = 14 B = 1111 = 15 C_in = 1  C_out = 1  Sum = 1110 = 14 {C_out, Sum} = 30
# Time = 30 ns A = 1111 = 15 B = 1111 = 15 C_in = 0  C_out = 1  Sum = 1110 = 14 {C_out, Sum} = 30
# Time = 35 ns A = 0110 = 6  B = 1001 = 9  C_in = 1  C_out = 1  Sum = 0000 = 0  {C_out, Sum} = 16
# Finished simulation at 40 ns.
```



**Change RADIX to
UNSIGNED
(not Decimal:
Signed)**

 Example 3: 4-bit Binary Adder (v2)

- Verilog dataflow description of a 4-bit binary adder using hard literals:



- Design Entry:


```
// Dataflow model of a 4-bit Binary Adder (v2)
module BinAdder_4bit_v2 (
    input    [3:0] A, B,
    input    C_in,
    output   [3:0] Sum,
    output   C_out
);

    // internal signal
    wire [4:0] sum_temp;

    assign sum_temp = {1'b0, A} + {1'b0, B} + {4'b0000, C_in};
    assign Sum      = sum_temp[3:0];
    assign C_out    = sum_temp[4];
endmodule
```

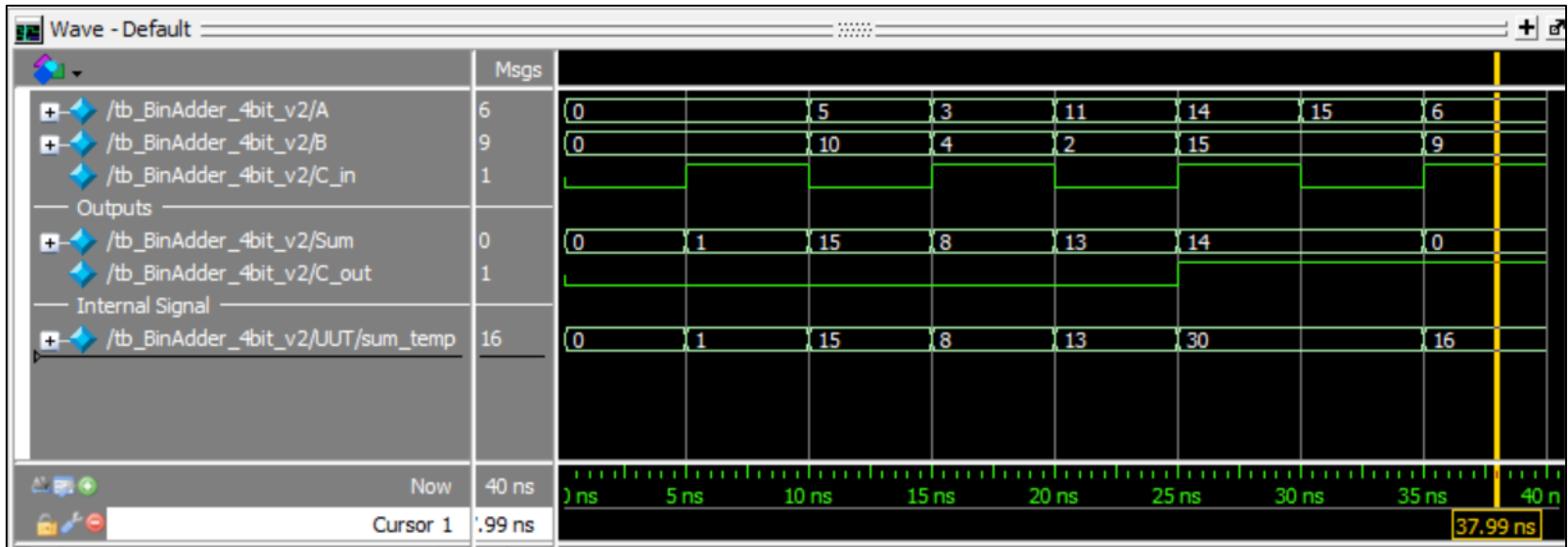Example 3: Simulation (Binary Adder v2)

```
# Starting simulation at 0 ns...
# Time = 0 ns  A = 0000 = 0  B = 0000 = 0  C_in = 0  C_out = 0  Sum = 0000 = 0  {C_out, Sum} = 0
# Time = 5 ns  A = 0000 = 0  B = 0000 = 0  C_in = 1  C_out = 0  Sum = 0001 = 1  {C_out, Sum} = 1
# Time = 10 ns A = 0101 = 5  B = 1010 = 10 C_in = 0  C_out = 0  Sum = 1111 = 15 {C_out, Sum} = 15
# Time = 15 ns A = 0011 = 3  B = 0100 = 4  C_in = 1  C_out = 0  Sum = 1000 = 8  {C_out, Sum} = 8
# Time = 20 ns A = 1011 = 11 B = 0010 = 2  C_in = 0  C_out = 0  Sum = 1101 = 13 {C_out, Sum} = 13
# Time = 25 ns A = 1110 = 14 B = 1111 = 15 C_in = 1  C_out = 1  Sum = 1110 = 14 {C_out, Sum} = 30
# Time = 30 ns A = 1111 = 15 B = 1111 = 15 C_in = 0  C_out = 1  Sum = 1110 = 14 {C_out, Sum} = 30
# Time = 35 ns A = 0110 = 6  B = 1001 = 9  C_in = 1  C_out = 1  Sum = 0000 = 0  {C_out, Sum} = 16
# Finished simulation at 40 ns.
```



Change RADIX to UNSIGNED

Constants


- Constant values are frequently found in **expressions and array boundaries**
- Fixed within the module and can't be modified
- **Good design practice:** **replace “hard literals” with symbolic constants**
- Declared using the ***localparam*** keyword (*local parameter*)
- Examples:

```
localparam      DATA_WIDTH = 8,  
                  DATA_RANGE = 2**DATA_WIDTH - 1;
```

```
localparam      UART_PORT      = 4'b0001,  
                  LCD_PORT       = 4'b0010,  
                  MOUSE_PORT     = 4'b0100;
```

 
Example 4: 4-bit Binary Adder (v3)

- Verilog dataflow description of a 4-bit binary adder using constants (localparam):



```

// Dataflow model of a 4-bit Binary Adder (v3)
// using constants (localparam)
//
module BinAdder_4bit_v3 (
    input      [3:0] A, B,
    input      C_in,
    output     [3:0] Sum,
    output     C_out
);

// constant declarations
localparam N = 4;

// internal signal
wire [N:0] sum_temp;

assign sum_temp = {1'b0, A} + {1'b0, B} + {4'b0000, C_in};
assign Sum      = sum_temp[N-1:0];
assign C_out    = sum_temp[N];
endmodule
  
```

Useful for allowing the Verilog code to be easily modified
(i.e., changing the design to an 8-bit adder, etc.)

Parameters

- A Verilog module can be **instantiated as a component** and becomes a part of a larger design (*through structural modeling*)
- ***Parameter*** is **another way of declaring constants**, which passes that constant value to a module
- **Cannot be modified inside the module** (*acts like a constant*)
 - Functions like a “**global**” version of a ***localparam*** (*constant*)
- **Default value** must be set inside the module but can be overridden once the design is synthesized
- This makes the module **versatile, reusable, and scalable**


Parameters

- Syntax:

```
module [module_name]
    #( parameter [parameter_name] = [default_value];
        ...
        parameter [parameter_name] = [default_value];
    )
    ( // Port declarations
    );
```

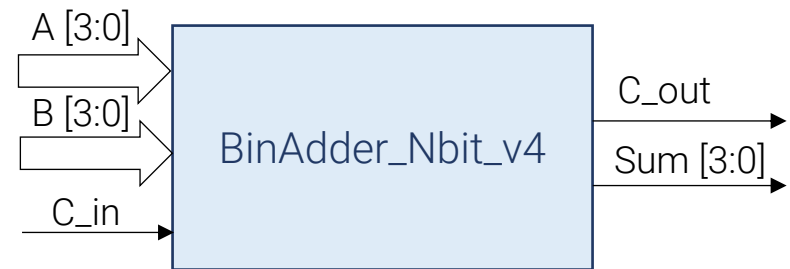Example 5: 4-bit Binary Adder (v4)

- Verilog dataflow description of a 4-bit binary adder using parameters:



```

// Dataflow model of a N-bit Binary Adder (v4)
// using parameters
//
module BinAdder_Nbit_v4
  #(parameter N = 4) // default value = 4
  (
    input  [N-1:0] A, B,
    input          C_in,
    output [N-1:0] Sum,
    output          C_out
  );

  // constant declarations
  // localparam here ...

  // internal signals
  wire [N:0] sum_temp;

  assign sum_temp = {1'b0, A} + {1'b0, B} + { {(N) {1'b0}}, C_in};
  assign Sum      = sum_temp[N-1:0];
  assign C_out    = sum_temp[N];
endmodule
  
```

Useful for allowing the Verilog code to be easily modified from outside the module (i.e., changing the design to an 8-bit adder, etc.)

Example 5: Testbench (Binary Adder v4)

```
// Testbench file of Dataflow Binary Adder (v4)
timescale 1 ns / 1 ps
module tb_BinAdder_Nbit_v4 ();

    // declare inputs as reg types
    reg [3:0] A, B;
    reg      C_in;

    // outputs as wire types
    wire [3:0] Sum;
    wire      C_out;

    // instantiate UUT
    BinAdder_Nbit_v4 #(N(4))
    UUT (.A(A), .B(B), .C_in(C_in), .Sum(Sum), .C_out(C_out));

    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);
        A = 4'd0; B = 4'd0; C_in = 1'b0; #5
        A = 4'd0; B = 4'd0; C_in = 1'b1; #5
        A = 4'd5; B = 4'd10; C_in = 1'b0; #5
        A = 4'd3; B = 4'd4; C_in = 1'b1; #5
        A = 4'd11; B = 4'd2; C_in = 1'b0; #5
        A = 4'd14; B = 4'd15; C_in = 1'b1; #5
        A = 4'd15; B = 4'd15; C_in = 1'b0; #5
        A = 4'd6; B = 4'd9; C_in = 1'b1; #5

        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial begin
        $monitor("Time = %2d ns\t A = %b\t B = %b\t C_in = %b\t C_out = %b\t Sum = %b\t {C_out, Sum} = %2d",
            $time, A, A, B, B, C_in, C_out, Sum, Sum, (Sum+(C_out*(16))) );
    end
endmodule
```

Useful for allowing the Verilog code to be easily modified from outside the module (in this case: from the testbench)


Example 5: Simulation (Binary Adder v4)

- Using $N = 4$: *4-bit Binary Adder*



Example 6: Reusing Parameterized Binary Adder

- Verilog structural description of *instantiating* the binary adders (v4):

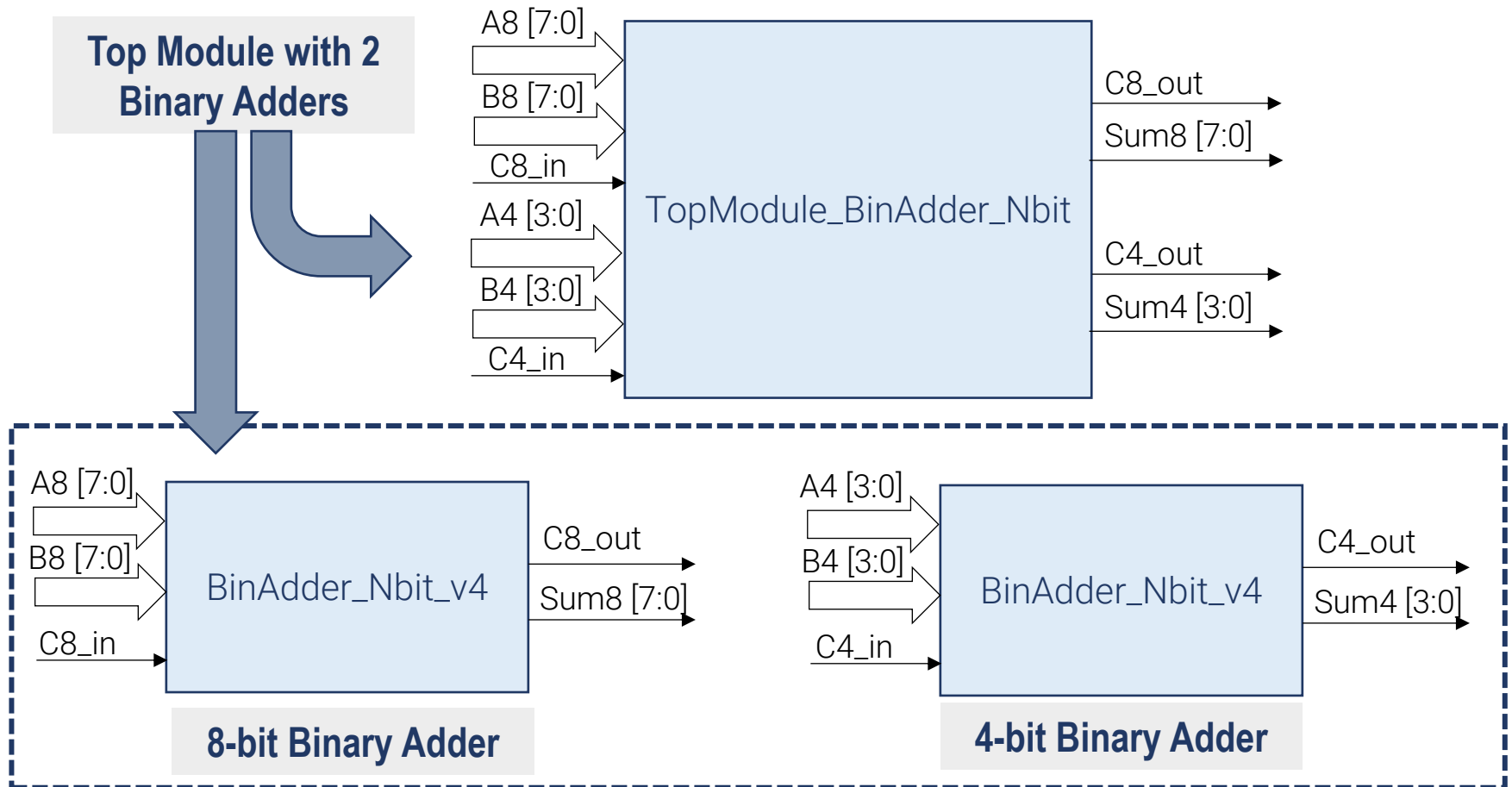

Example 6: Reusing Parameterized Binary Adder

- Verilog structural description of *instantiating* the binary adders (v4):


```

1 // Top Module instantiating 2 N-bit Binary Adders (v4)
2 //   using parameters
3 //
4 module TopModule_BinAdder_Nbit (
5     // ports for 4-bit Bin Adder
6     input    [3:0] A4, B4,
7     input    C4_in,
8     output   [3:0] Sum4,
9     output   C4_out,
10    // ports for 8-bit Bin Adder
11    input    [7:0] A8, B8,
12    input    C8_in,
13    output   [7:0] Sum8,
14    output   C8_out
15 );
16
17 // instantiate 8-bit adder
18 BinAdder_Nbit_v4 #( .N(8) )
19     Adder_8bit ( .A(A8), .B(B8), .C_in(C8_in), .Sum(Sum8), .C_out(C8_out) );
20
21 // instantiate 4-bit adder
22 BinAdder_Nbit_v4 #( .N(4) )
23     Adder_4bit ( .A(A4), .B(B4), .C_in(C4_in), .Sum(Sum4), .C_out(C4_out) );
24
25 endmodule
26
    
```

Useful for allowing the Verilog code to be easily modified from outside the module (in this case: from an external module)


Example 6: Synthesis (Parameterized Bin Adder)

- RTL Schematic View:

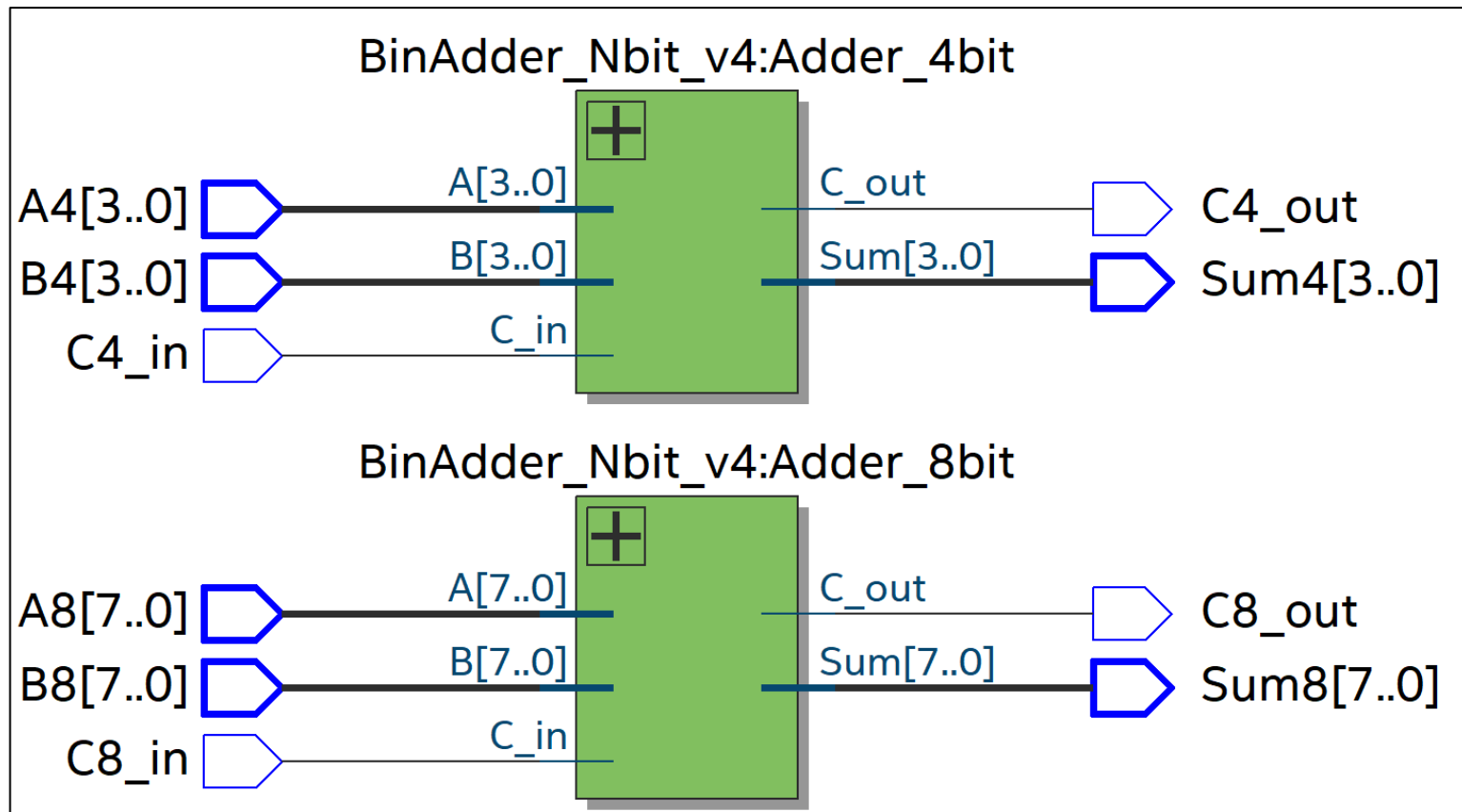

Example 6: Synthesis (Parameterized Bin Adder)

- RTL Schematic View:

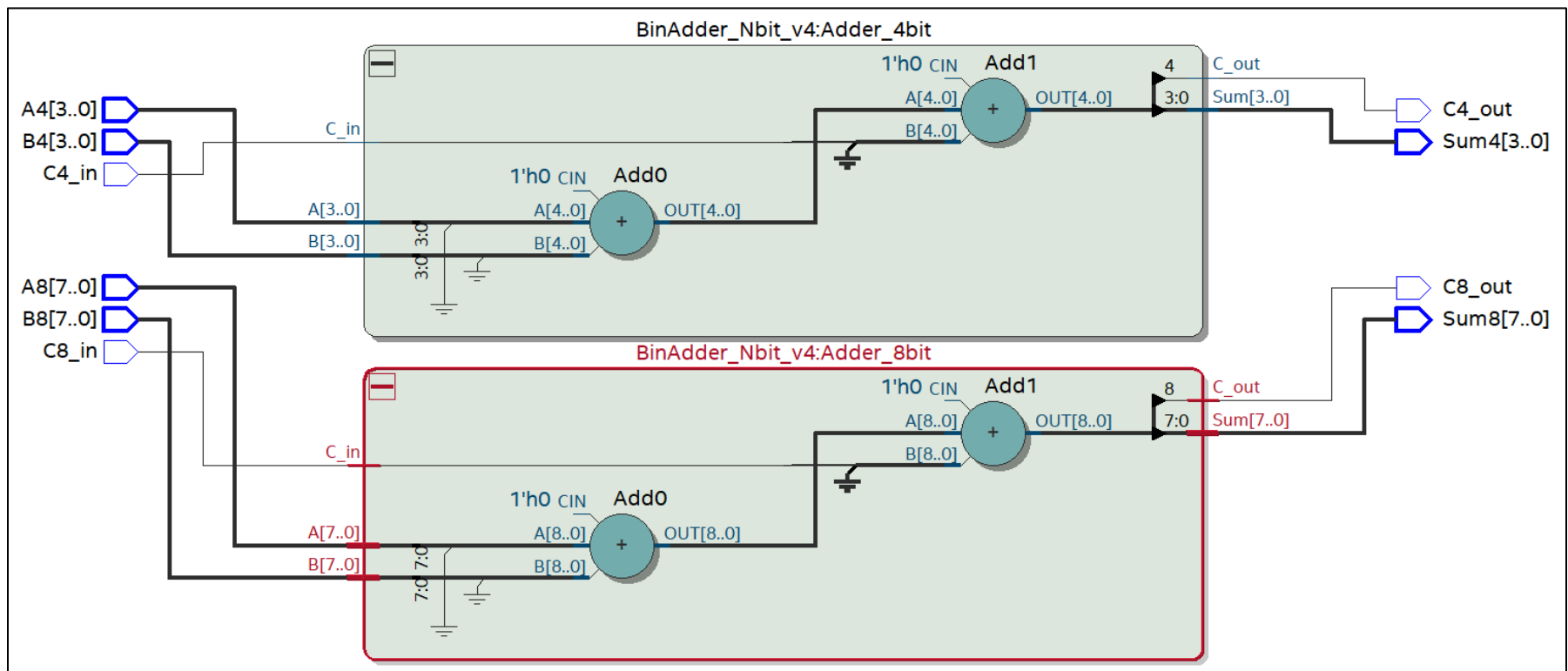



End of Unit 4