



University of San Carlos | Department of
COMPUTER ENGINEERING

CpE 3101L – Introduction to HDL

Unit 6: Behavioral Modeling of Sequential Circuits

Lecture 1

Outline

- Behavioral Modeling of Sequential Circuits
- *Always* Block and Sensitivity List
- Latches, Flip-flops, Registers, and Counters
- Non-blocking vs. Blocking Assignments
- Synchronous vs. Asynchronous Resets
- Combinational vs. Sequential Logic
- Guidelines for Good Synthesis of Sequential Circuits
- Simulation for Sequential Circuits

Behavioral Modeling of Sequential Circuits

- **Behavioral modeling** represents digital circuits at a functional and algorithmic level.
 - Involves describing at a **higher level of abstraction**
- Mostly used to describe sequential logic.
- **Behavioral HDL models** describe sequential circuits by their *behavior (functionality)*.

Always Block and Sensitivity List

- Behavioral descriptions uses **procedural assignment statements** with keyword *always*
 - *always* can also be used in **simulations** (together with *initial*)
 - *always* is **synthesizable** (unlike *initial*)
- Consists of a **sensitivity list** (*an event control expression*)
- **Sensitivity list** is a list of signals that is monitored for changes
 - Whenever **one of the signals** in the sensitivity list **changes its value**, the **statements inside the *always* block are evaluated sequentially**.

Always Block and Sensitivity List

- All signals assigned inside the *always* block must be declared as *reg*
- Contrary to a *wire* (a *net* data type), a *reg* retains its value until a new value is assigned (*variable* data type)

```
// declare reg here;
```

```
always @( [sensitivity_list] )  
begin  
    // local variable declarations here; (optional)  
  
    // body: composed of procedural statements;  
end
```


- Note: Use of **begin-end** are required when the contents of the *always* block have *more than one statement*

Latches, Flip-flops, and Registers

- Use of same behavioral construct (*always* block), but *change in sensitivity list*.
- All sequential circuits must have *clock signal*.
 - Latches and flip-flops differ in the clock sensitivity.
 - **Latches** are *level-sensitive (positive or negative level)*
 - **Flip-flops** are *edge-sensitive (positive/rising or negative/falling edge)*
- If D and Q are more than 1-bit wide, they are usually called **registers** and are *edge-sensitive*

 
Example 1: Positive-level D Latch

- Verilog behavioral description of a positive-level D latch:




```
// Positive-level triggered D Latch
// with Active High Reset
//
module D_Latch (
    input wire Clk, Reset, D,
    output reg Q
);

 // sensitivity list for a latch is similar
// to a combinational circuit
always @(*)
begin
    if (Reset)
        Q <= 1'b0;
    else
        if (Clk)
            Q <= D;
end
endmodule
```



- RTL Schematic View:

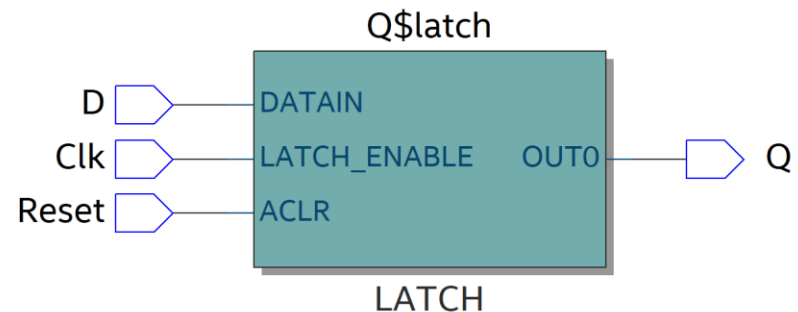

Example 1: Testbench File (D Latch)

```
// Testbench file of D Latch
timescale 1 ns / 1 ps
module tb_D_Latch ();

    // inputs as reg, outputs as wire
    reg  Clk, Reset, D;
    wire Q;

    // instantiate UUT
    D_Latch UUT ( .Clk(Clk), .Reset(Reset), .D(D), .Q(Q) );

    // set initial value for clock
    initial
        Clk = 1'b0;

    // clock generator
    always
        #5 Clk = ~Clk;    // toggles/complements the clock every after 5 ns

    // set reset value
    initial begin
        Reset = 1'b1; #10 // reset is initially enabled (active high)
        Reset = 1'b0;    // reset is disabled after 10 ns
    end

    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);
        D = 1'b0; #12 // set first delay before clock edge (every 5 ns)
        D = 1'b1; #25
        D = 1'b0; #10
        D = 1'b1; #12
        D = 1'b0; #10
        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial
        $monitor("Time = %2d ns\t Clk = %b\t Reset = %b\t D = %b\t Q = %d", $time, Clk, Reset, D, Q);

endmodule
```

 

Example 1: Simulation (D Latch)

- Standard Output:

Clk 
Response to positive level


```
# Starting simulation at 0 ns...
# Time = 0 ns Clk = 0 Reset = 1 D = 0 Q = 0
# Time = 5 ns Clk = 1 Reset = 1 D = 0 Q = 0
# Time = 10 ns Clk = 0 Reset = 0 D = 0 Q = 0
# Time = 12 ns Clk = 0 Reset = 0 D = 1 Q = 0
# Time = 15 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 20 ns Clk = 0 Reset = 0 D = 1 Q = 1
# Time = 25 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 30 ns Clk = 0 Reset = 0 D = 1 Q = 1
# Time = 35 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 37 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Time = 40 ns Clk = 0 Reset = 0 D = 0 Q = 0
# Time = 45 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Time = 47 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 50 ns Clk = 0 Reset = 0 D = 1 Q = 1
# Time = 55 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 59 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Time = 60 ns Clk = 0 Reset = 0 D = 0 Q = 0
# Time = 65 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Finished simulation at 69 ns.
```

- Waveform:



 Example 2: Positive-edged D Flip-flop



- Verilog behavioral description of a positive-edged D flip-flop:



```
// Positive-edged triggered D Flip-flop
// with Active High Reset
//
module D_FF (
    input wire    Clk, Reset, D,
    output reg    Q
);

always @(posedge Clk)
begin
    if (Reset)
        Q <= 1'b0;
    else
        Q <= D;
end
endmodule
```

  If negative-edged triggered:
always @ (negedge Clk)



See the difference in the sensitivity list

Example 2: Testbench File (D F/F)

```
// Testbench file of D Flip-flop
timescale 1 ns / 1 ps
module tb_D_FF ();

    // inputs as reg, outputs as wire
    reg  Clk, Reset, D;
    wire Q;

    // instantiate UUT
    D_FF UUT ( .Clk(Clk), .Reset(Reset), .D(D), .Q(Q) );

    // set initial value for clock
    initial
        Clk = 1'b0;

    // clock generator
    always
        #5 Clk = ~Clk;    // toggles/complements the clock every after 5 ns

    // set reset value
    initial begin
        Reset = 1'b1;    #10 // reset is initially enabled (active high)
        Reset = 1'b0;    // reset is disabled after 10 ns
    end


    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);
        D = 1'b0;    #12 // set first delay before clock edge (every 5 ns)
        D = 1'b1;    #25
        D = 1'b0;    #10
        D = 1'b1;    #12
        D = 1'b0;    #10
        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial
        $monitor("Time = %2d ns\t Clk = %b\t Reset = %b\t D = %b\t Q = %b", $time, Clk, Reset, D, Q);

endmodule
```


Example 2: Simulation (D F/F)

- Standard Output:

 


```
# Starting simulation at 0 ns...
# Time = 0 ns Clk = 0 Reset = 1 D = 0 Q = x
# Time = 5 ns Clk = 1 Reset = 1 D = 0 Q = 0
# Time = 10 ns Clk = 0 Reset = 0 D = 0 Q = 0
# Time = 12 ns Clk = 0 Reset = 0 D = 1 Q = 0
# Time = 15 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 20 ns Clk = 0 Reset = 0 D = 1 Q = 1
# Time = 25 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 30 ns Clk = 0 Reset = 0 D = 1 Q = 1
# Time = 35 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 37 ns Clk = 1 Reset = 0 D = 0 Q = 1
# Time = 40 ns Clk = 0 Reset = 0 D = 0 Q = 1
# Time = 45 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Time = 47 ns Clk = 1 Reset = 0 D = 1 Q = 0
# Time = 50 ns Clk = 0 Reset = 0 D = 1 Q = 0
# Time = 55 ns Clk = 1 Reset = 0 D = 1 Q = 1
# Time = 59 ns Clk = 1 Reset = 0 D = 0 Q = 1
# Time = 60 ns Clk = 0 Reset = 0 D = 0 Q = 1
# Time = 65 ns Clk = 1 Reset = 0 D = 0 Q = 0
# Finished simulation at 69 ns.
```

- Waveform:

 


Compare Waveforms

Positive-level triggered D Latch

 

Positive-edged triggered D Flip-flop

 

Non-blocking Assignment

- Uses **<= operator** in assigning values in a *reg* (inside an *always* block)
- Executes all statements in the *always* block concurrently
- Evaluated and assigned in two steps:
 - The right-hand side is evaluated immediately.
 - The assignment to the left-hand side is postponed until other evaluations in the current time step are completed
- Non-blocking assignment should be used in sequential logic

```
// Positive-edged triggered D Flip-flop
// with Active High Reset
//
module D_FF (
    input wire  C1k, Reset, D,
    output reg  Q
);

    always @(posedge C1k)
    begin
        if (Reset)
            Q <= 1'b0;
        else
            Q <= D;
    end
endmodule
```

Blocking vs. Non-blocking

- Blocking Assignment (=)
 - Used in combinational logic

```
// using blocking statements
reg x, y;
always @ (*)
begin
    x = a & b;
    y = x | c;
end
```

Execution:

1. x is evaluated
2. y is evaluated using value from (1)

- Non-blocking Assignment (<=)
 - Used in sequential logic

```
// using non-blocking statements
reg x, y;
always @ (*)
begin
    x <= a & b;
    y <= x | c;
end
```

****This example is for illustration and discussion purposes only.***
Combinational logic should always use blocking assignments (=).

Execution:

1. (a & b) is evaluated
2. (x | c) is evaluated
3. (1) is assigned to x, (2) is assigned to y (concurrent assignments)

Reset

- It is common practice to have a **reset** signal for easy initialization.
- **Reset signal** is usually low-asserted (active-low) by convention.
- Synthesis tools usually have strict format flip-flops.
- Two types: synchronous and asynchronous resets

Synchronous vs. Asynchronous Reset



See the difference in the sensitivity lists

```
// Positive-edged triggered D Flip-flop
// with Active Low Reset
//
module D_FF_SyncReset (
    input wire  Clk, nReset, D,
    output reg  Q
);

// Synchronous Active Low Reset
always @(posedge Clk) begin
    if (!nReset)
        Q <= 1'b0;
    else
        Q <= D;
end
endmodule
```

```
// Positive-edged triggered D Flip-flop
// with Active Low Reset
//
module D_FF_AsyncReset (
    input wire  Clk, nReset, D,
    output reg  Q
);

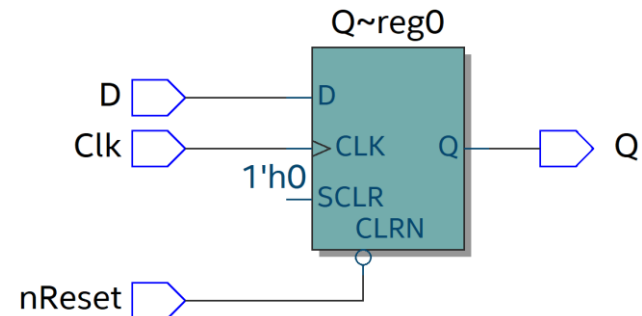 // Asynchronous Active Low Reset
always @(posedge Clk, negedge nReset) begin
    if (!nReset)
        Q <= 1'b0;
    else
        Q <= D;
end
endmodule
```



If active high Reset: `always @ (... , posedge Reset)`

Similar Testbench Files

```
// Testbench file of D Flip-flop
timescale 1 ns / 1 ps
module tb_D_FF_SyncReset ();

    // inputs as reg, outputs as wire
    reg  Clk, nReset, D;
    wire Q;

    // instantiate UUT
    D_FF_SyncReset UUT ( .Clk(Clk), .nReset(nReset), .D(D), .Q(Q) );

    // set initial value for clock
    initial Clk = 1'b0;

    // clock generator
    always #5 Clk = ~Clk;    // toggles/complements the clock every after 5 ns

    // set reset value
    initial begin
        nReset = 1'b1; #4    // reset is initially disabled
        nReset = 1'b0; #10   // reset is enabled after 4 ns (active low)
        nReset = 1'b1; #25   // reset is then disabled after 10 ns
        nReset = 1'b0; #10   // reset is enabled after 25 ns
        nReset = 1'b1;      // reset is then disabled again after 10 ns
    end


    // generate stimuli
    initial begin
        $display("Starting simulation at %0d ns...", $time);
        D = 1'b1;    #12    // set first delay before clock edge (every 5 ns)
        D = 1'b0;    #15
        D = 1'b1;    #10
        D = 1'b0;    #10
        D = 1'b1;    #25
        $display("Finished simulation at %0d ns.", $time);
        $stop;
    end

    // response monitor
    initial $monitor("Time = %2d ns\t Clk = %b\t nReset = %b\t D = %b\t Q = %b", $time, Clk, nReset, D, Q);
endmodule
```


The only differences are the names.

Compare Waveforms

Synchronous (Active Low) Reset

 

Asynchronous (Active Low) Reset

 


Enable

- Many circuits require a **flip-flop** or **register** to hold a value for more than a clock cycle, controlled by an **enable** signal.
- In Verilog, an incompletely-specified **if-else** and **case** statements produce a **latch**.


```
// Positive-edged triggered D Flip-flop
// with Active High Enable
//
module D_FF_Enable (
    input wire Clk, nReset, D, En,
    output reg Q
);

 // Synchronous Active Low Reset
always @(posedge Clk) begin
    if (!nReset)
        Q <= 1'b0;
    else
        if (En)
            Q <= D;
        // no "else" here produces a latch
end
endmodule
```




Incorporating Logic
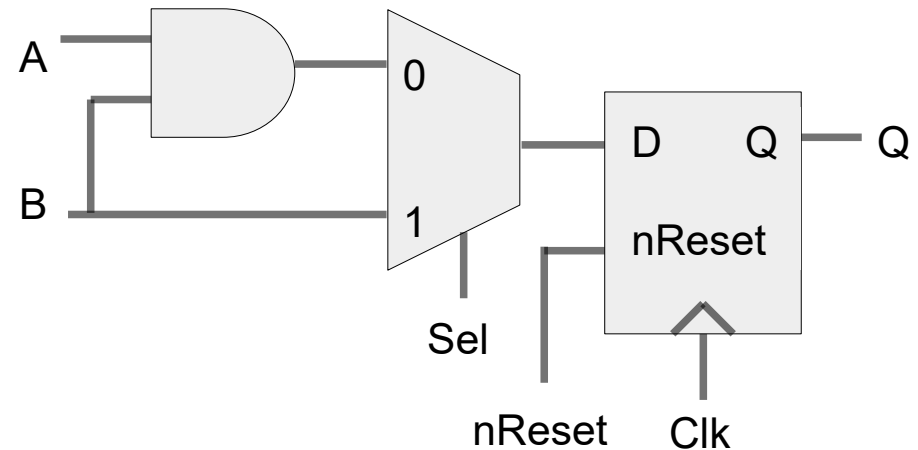
```
// Synchronous Active Low Reset
...
always @(posedge Clk)
begin
    if (!nReset)
        Q <= 1'b0;
    else
        if (Sel)
            Q <= B;
        else
            Q <= A & B;
    end
...
```




Blocking vs. Non-blocking Assignments

```
// blocking assignments
// positive-edge triggered Clk
reg x, y;
always @(posedge Clk) begin
    x = a & b;
    y = x | c;
end
```

 


```
// non-blocking assignments
// positive-edge triggered Clk
reg y;
always @(posedge Clk) begin
    x <= a & b;
    y <= x | c;
end
```

 


Combinational vs. Sequential Logic

```
// combinational logic uses
// blocking assignments
reg x, y;
always @(*) begin
    x = a & b;
    y = x | c;
end
```

 


```
// sequential logic uses
// non-blocking assignments
reg y;
always @(posedge Clk) begin
    y <= (a & b) | c;
end
```

 


Example 3: 4-bit Binary Counter

- Verilog behavioral description of a 4-bit binary counter with parallel load:

| Clear | CLK | Load | Count | Function |
|-------|-----|------|-------|-------------------------|
| 0 | X | X | X | Clear to 0 |
| 1 | ↑ | 1 | X | Load inputs |
| 1 | ↑ | 0 | 1 | Count next binary state |
| 1 | ↑ | 0 | 0 | No change |

 

Example 3: 4-bit Binary Counter

 

| Clear | CLK | Load | Count | Function |
|-------|-----|------|-------|-------------------------|
| 0 | X | X | X | Clear to 0 |
| 1 | ↑ | 1 | X | Load inputs |
| 1 | ↑ | 0 | 1 | Count next binary state |
| 1 | ↑ | 0 | 0 | No change |

```

module Binary_Counter_4_Par_Load (
    output reg [3: 0]      A_count,    // Data output
    output                C_out,      // Output carry
    input [3: 0]          Data_in,    // Data input
    input                 Count,      // Active high to count
                                Load,  // Active high to load
                                CLK,    // Positive-edge sensitive
                                Clear_b // Active low
);
assign C_out = Count && (~Load) && (A_count == 4'b1111);
always @ (posedge CLK, negedge Clear_b)
    if (~Clear_b)      A_count <= 4'b0000;
    else if (Load)      A_count <= Data_in;
    else if (Count)     A_count <= A_count + 1'b1;
    else                A_count <= A_count; // redundant statement
endmodule

```

Synthesis of Sequential Elements

- For most synthesis tools, an *always* block with a **posedge** or **negedge** in the sensitivity list will create a **flip-flop** (*clock automatically set by **posedge** or **negedge***).

Guidelines for Good Synthesis

- Use non-blocking assignments (\leq) to model sequential circuits.
 - It may be fine to use blocking statements, but it is NOT recommended if you do not know what you are doing.
 - The hardware generated by non-blocking assignments is independent of the ordering of the assignments.
- Do not mix blocking and non-blocking assignments in the same *always* block.
- Do not make assignments to the same variable from more than one *always* block.
 - It is a Verilog race condition, even when using non-blocking assignments.



End of Unit 6